

ECE385 Experiment #5

Eric Meyers, Ryan Helsdingen

Section ABG; TAs: Ben Delay, Shuo Liu

February 17th, 2016

emeyer7, helsdin2

- I. INTRODUCTION
- II. 8-BIT MULTIPLICATION EXAMPLE
- III. DESCRIPTION OF CIRCUIT
- IV. SCHEMATIC/BLOCK DIAGRAM
- V. PRE-LAB SIMULATION WAVEFORMS
- VI. POST LAB
- VII. CONCLUSION

VIII. FIGURES