

EXPERIMENT #6


Simple Computer SLC-3.2 in Systemverilog

I. OBJECTIVE

In this experiment, you will design a simple microprocessor using SystemVerilog. It will be a subset of the LC-3 ISA, a 16-bit processor with 16-bit Program Counter (PC), 16-bit instructions, and 16-bit registers. (*For LC-3, see Patt and Patel (ECE 120 textbook).*)

II. INTRODUCTION

There are three main components to the design of a processor. The central processing unit (CPU), the memory that stores instructions and data, and the input/output interface that communicates with external devices. You will be provided with the interface between the CPU and the memory (memory read and write functions). The computer will first fetch an instruction from the memory, decode it to determine the type of the instruction, execute the instruction, and then fetch again. See Figure 1.

 **Figure 1**

The CPU will contain a PC, a Instruction Register (IR), a Memory Address Register (MAR), a Memory Data Register (MDR), a Instruction Sequencer/Decoder, a status register (nzp), a 8x16 general-purpose register file, and an Arithmetic Logic Unit (ALU). All registers and instructions are 16-bits wide. The ALU will operate on 16-bit inputs. The Instruction Sequencer/Decoder will be responsible for providing proper control signals to the other components of the processor. It will contain a state machine that will provide the signals that will control the sequence of operations (fetch → decode → execute → fetch next) in the processor.

The simple computer will perform various operations based on the opcodes. An opcode specifies the operation to be performed. Specific opcodes and operations are shown in Table 1. The 4-bit opcode is specified by Instruction[15:12]; the remaining twelve bits contain data relevant that instruction.

In the table below, R(X) specifies a register in the register file, addressed by the three-bit address X. SEXT(X) indicates the 2's complement sign extension of the operand X to 16 bits. nzp is the status register mentioned above. It is a three-bit value that states whether the resulting value loaded to the register file is negative, zero, or positive. This must be updated whenever an instruction performs a write to the register file (except JSR). For all instructions, $PC \leftarrow PC + 1$ is implicit, unless PC is stated to get some other value. In the table, right-hand-side "PC" indicates the value of the PC register after it was incremented immediately following fetch.

| Instruction | Instruction(15 downto 0) | | | | | | | Operation |
|-------------|--------------------------|-----------|------------|---------|-----------|-----|--|---|
| ADD | 0001 | DR | SR1 | 0 | 00 | SR2 | | $R(DR) \leftarrow R(SR1) + R(SR2)$ |
| ADDi | 0001 | DR | SR | 1 | imm5 | | | $R(DR) \leftarrow R(SR) + \text{SEXT}(\text{imm5})$ |
| AND | 0101 | DR | SR1 | 0 | 00 | SR2 | | $R(DR) \leftarrow R(SR1) \text{ AND } R(SR2)$ |
| ANDi | 0101 | DR | SR | 1 | imm5 | | | $R(DR) \leftarrow R(SR) \text{ AND } \text{SEXT}(\text{imm5})$ |
| NOT | 1001 | DR | SR | 111111 | | | | $R(DR) \leftarrow \text{NOT } R(SR)$ |
| BR | 0000 | N | Z | P | PCOffset9 | | | if ((nzp AND NZP) != 0) PC \leftarrow PC + SEXT(PCOffset9) |
| JMP | 1100 | 000 | | BaseR | 000000 | | | PC \leftarrow R(BaseR) |
| JSR | 0100 | 1 | PCOffset11 | | | | | R(7) \leftarrow PC; PC \leftarrow PC + SEXT(PCOffset11) |
| LDR | 0110 | DR | BaseR | offset6 | | | | $R(DR) \leftarrow M[R(\text{BaseR}) + \text{SEXT}(\text{offset6})]$ |
| STR | 0111 | SR | BaseR | offset6 | | | | $M[R(\text{BaseR}) + \text{SEXT}(\text{offset6})] \leftarrow R(SR)$ |
| PAUSE | 1101 | ledVect12 | | | | | | LEDs \leftarrow ledVect12; Wait on Continue |

Table 1: The SLC-3.2 ISA

The IR will provide the Instruction Sequencer/Decoder with the instruction to be executed. The IR will also provide the datapath with any other necessary data. As mentioned earlier, the Instruction Sequencer/Decoder will need to generate the control signals to execute the instructions in proper order. The Instruction Sequencer/Decoder will also specify the operation

to the ALU (e.g. add, etc.). Note that each operation will take multiple cycles and the Instruction Sequencer/Decoder will need to provide signals appropriately at each cycle.

On a reset, the Instruction Sequencer/Decoder should reset to the starting “halted” state, and wait for Run to go high. The PC should be reset to zero upon a reset, where it should proceed on incrementing itself when Run is pressed for fetching the instructions line by line. The first three lines of instructions will be used to load the PC with the value on the slider switches, which indicates the starting address of the instruction(s) of interest (in the form of test programs for the demo), and the program should begin executing instructions starting at the PC. Your computer must be able to return to the halted state any time a reset signal arrives.

Instruction Summary

| | |
|-------|--|
| ADD | Adds the contents of SR1 and SR2, and stores the result to DR. Sets the status register. |
| ADDi | Add Immediate. Adds the contents of SR to the sign-extended value imm5, and stores the result to DR. Sets the status register. |
| AND | ANDs the contents of SR1 with SR2, and stores the result to DR. Sets the status register. |
| ANDi | And Immediate. ANDs the contents of SR with the sign-extended value imm5, and stores the result to DR. Sets the status register. |
| NOT | Negates SR and stores the result to DR. Sets the status register. |
| BR | Branch. If any of the condition codes match the condition stored in the status register, takes the branch; otherwise, continues execution. (An unconditional jump can be specified by setting NZP to 111.) Branch location is determined by adding the sign-extended PCOffset9 to the PC. |
| JMP | Jump. Copies memory address from BaseR to PC. |
| JSR | Jump to Subroutine. Stores current PC to R(7), adds sign-extended PCOffset11 to PC. |
| LDR | Load using Register offset addressing. Loads DR with memory contents pointed to by (BaseR + SEXT(offset6)). Sets the status register. |
| STR | Store using Register offset addressing. Stores the contents of SR at the memory location pointed to by (BaseR + SEXT(offset6)). |
| PAUSE | Pauses execution until Continue is asserted by the user. Execution should only unpause if Continue is asserted during the current pause instruction; that is, when multiple pause instructions are encountered, only one should be “cleared” per press of Continue. While paused, ledVect12 is displayed on the board LEDs. See I/O Specification section for usage notes. |

Here are the operations in more detail:

Fetch:

$MAR \leftarrow PC$; MAR = memory address to read the instruction from

$MDR \leftarrow M(MAR)$; MDR = Instruction read from memory (note that M(MAR) specifies the data at address MAR in memory).

$IR \leftarrow MDR$; IR = Instruction to decode
 $PC \leftarrow (PC + 1)$

Decode:

Instruction Sequencer/Decoder $\leftarrow IR$

Execute:

Perform the operation based on the signals from the Instruction Sequencer/Decoder and write the result to the destination register or memory.

Fetch, Load, and Store Operations:

For Fetch, Load, and Store operations you will need to set the memory signals appropriately for each state of the fetch/load/store sequence. You should incorporate the three-state Fetch, Load, and Store operations in your main Instruction Sequencing State Diagram.

FETCH:

state1: $MAR \leftarrow PC$
 state2: $MDR \leftarrow M(MAR)$; -- *assert Read Command on the RAM*
 state3: $IR \leftarrow MDR$;
 $PC \leftarrow PC+1$; -- "+1" inserts an incrementer/counter instead of an adder.
 Go to the next state.

LOAD:

state1: $MAR \leftarrow (BaseR + SEXT(offset6))$ from ALU
 state2: $MDR \leftarrow M(MAR)$; -- *assert Read Command on the RAM*
 state3: $R(DR) \leftarrow MDR$;

STORE:

state1: $MAR \leftarrow (BaseR + SEXT(offset6))$ from ALU; $MDR \leftarrow R(SR)$
 state2: $M(MAR) \leftarrow MDR$; -- *assert Write Command on the RAM*

Memory Interface

The DE2 board is equipped with one 512-KB SRAM. You will need to provide a memory address in MAR, data to be written in MDR (in the case of Store), and the Read and Write signals. The interface for these memory chips is as follows:

| | |
|-----|---|
| I/O | Bidirectional 16-bit data bus. |
| A | 18-bit Address bus (shared between both chips) |
| CE | Chip Enable. When active, allows read/write operations. Active low. |
| UB | Upper Byte enable. Allows read/write operations on I/O<15:8>. Active low. |
| LB | Lower Byte enable. Allows read/write operations on I/O<7:0>. Active low. |
| OE | Output Enable. When active, RAM chips will drive output on selected banks of selected chips. Active low. |
| WE | Write Enable. When active, orders writes to selected banks of selected chips. Active low. Has priority over OE. |

Note that I/O is declared as an **inout** port type. This means that it is a bidirectional data bus. In general, any port that attempts to both read and write to a bus needs to be declared as an inout type. A port can write to the bus through an output port. When not writing to the bus, you should assign the output a high-impedance value (“ZZZZZZZZZZZZZZZZZZ”). Otherwise, when reading from memory, both your circuit and the SRAM will try to drive the line at the same time, with unpredictable results (possibly including damage to one or both chips). This functionality should be included in a separate entity that you should name “tristate_buffer”. This will have two inputs, the data from MDR and a select bit from the controller, and one output that you should tie to the data line. Reading from the data line requires no extra circuitry; the data line can be tied directly to the MDR input (multiplexed with MDR’s other sources).

I/O Specifications

I/O for this CPU is memory-mapped. I/O devices are connected to the memory signals, with a special buffer inserted on the memory data bus. When a memory access occurs at an I/O device address, the I/O device detects this, and sends a signal to the buffer to deactivate the memory, and instead use the I/O device’s data for the response. You will be provided with a SystemVerilog entity that encapsulates this functionality into a single module for you to insert between your processor and the external memory (this is part of what the mem2io module does) (see figures 2 & 3)

Mem2IO


This manages all I/O with the DE2 physical I/O devices, namely, the switches and 7-segment displays. See Table 2. Note that the two devices share the same memory address. This is acceptable, because one of the devices (the switches) is purely input, while the other (the hex displays) is purely output.

| Physical I/O Device | Type | Memory Address | “Memory Contents” |
|-----------------------|--------|----------------|-------------------|
| DE2 Board Hex Display | Output | 0xFFFF | Hex Display Data |
| DE2 Board Switches | Input | 0xFFFF | Switches(15:0) |

Table 2: Physical I/O Device List

You will need to create a top-level port map file that includes your CPU, the Mem2IO entity, and four HexDrivers. The CPU is a high level entity that contains the majority of your modules, including the ISDU. The various memory control signal inputs and the memory address input should be connected to the corresponding outputs from the CPU (which are also output from your top-level entity to the actual memory). The memory data inout port from your

CPU should be connected to the Data_CPU inout port of the Mem2IO unit; the Data_Mem inout port of the Mem2IO unit should be connected to an inout port on your top-level entity, which should be assigned to the appropriate pin connected to physical memory. The four “HEX#” output signals should be connected to HexDriver inputs. See the partial block diagrams in figures 2 & 3.

 

**Figure 2: Conceptual
Picture of Memory**

 


Figure 3: Memory with Mem2IO unit

Usage of the Pause Instruction

The Pause instruction is to be used in conjunction with I/O. Pausing allows the user time to set the switches before an input operation, and read the output after an output operation. The top two bits of the ledVect12 field of the instruction indicate the related I/O operation as indicated in Table 3. Note that these should be considered as masks, not as mutually exclusive values. For example, a ledVect12[11:10] value of “11” would indicate that both new data is being displayed on the hex displays and the program is asking for a new switch value. The remaining ledVect12 bits should be used to output a unique identifier to communicate the location in the program to keep track of the computer’s progress. NOTE: The ledVect12 vector does not mean anything to the processor; their sole purpose is to be a visual cue that the user can define (when programming) so that he/she can tell where the program is during execution. The following table reflects the convention used in the test programs.

| ledVect12(11:10) Mask | Meaning (cue for the user only) |
|------------------------------|---|
| “01” | Previous operation was a write to the hex display |
| “10” | Next operation is a read from switches |

Table 3: ledVect12(11:10) Masks for Pause Instruction

Your top-level circuit should have **at least** the following inputs and outputs:

Inputs

S – logic [15:0]
 Clk, Reset, Run, Continue –logic

Outputs


LED – logic [11:0]
 HEX0, HEX1, HEX2, HEX3 - logic [6:0]
 CE, UB, LB, OE, WE –logic
 ADDR – logic [19:0]

Bidirectional ports (inout)

Data - logic [15:0]

(You may expand this list as needed for simulation and debugging.)

SIMPLIFIED SAMPLE CPU BLOCK DIAGRAM

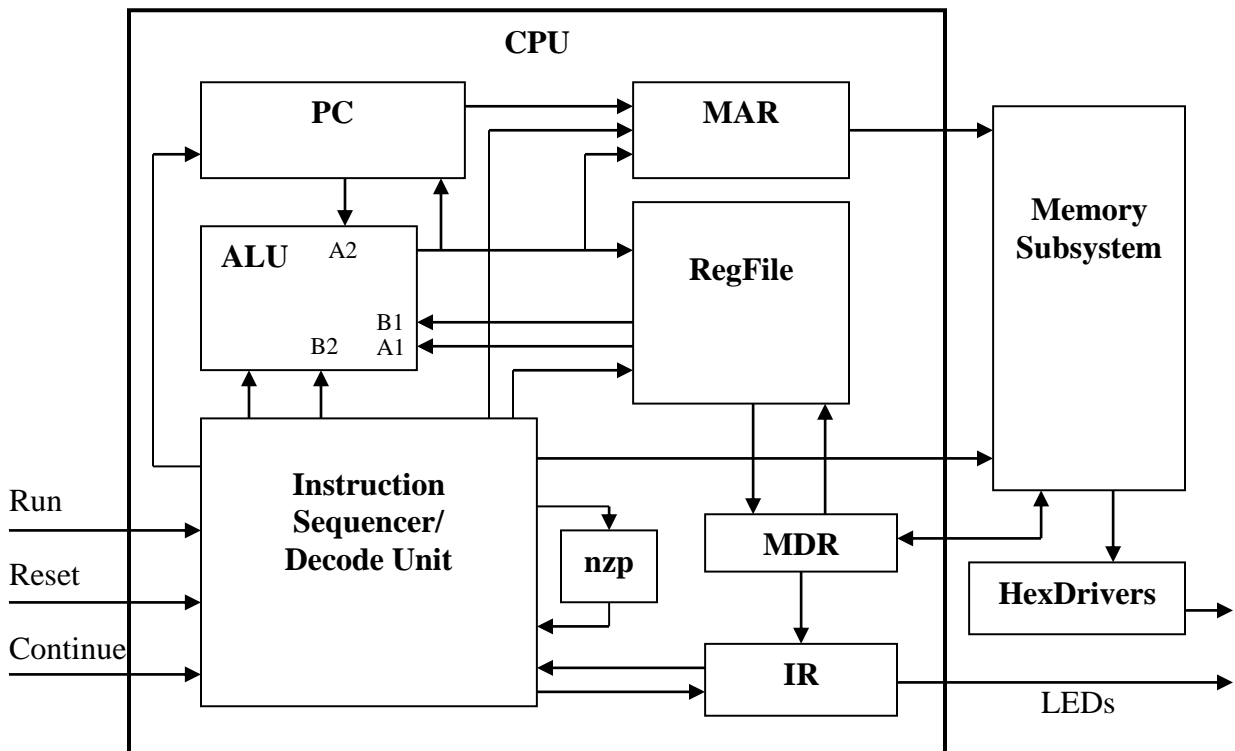

Notes: Arrows are shown for connections between components. There may be multiple signals going from one block to the other even if there is only one connection shown between the blocks. One arrow does not mean one signal/bus in all cases. Signal multiplexing has been omitted (your diagram should show a mux in front of most registers). All registers will also have Clk as an input. Note that this block diagram does not show the mem2io module

that should serve as an interface between the CPU and the memory (it is implicit in the memory subsystem block, this is just a reminder that you need to include it).

LC3 STATE DIAGRAM FROM APPENDIX C OF PATT AND PATEL

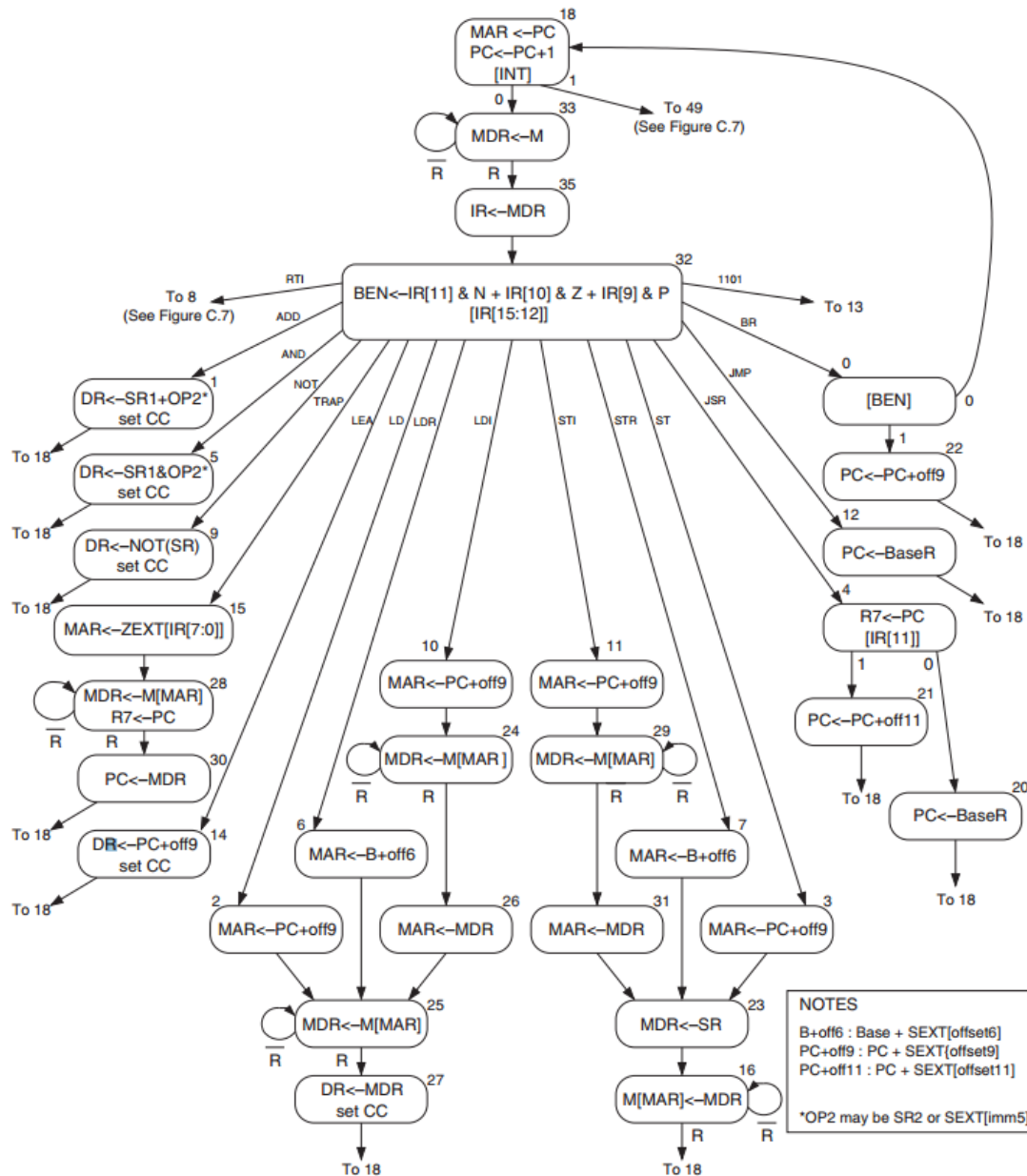


Figure C.2 A state machine for the LC-3

Notes: This is not the state diagram for the simplified LC3, it has some instructions that are not required to be implemented in this lab. Please refer to the instruction summary for details on which instructions are required to complete the lab.

III. PRE-LAB

A. **Week 1:**

Lab 6 is split up into two discrete tasks. In the first week, you will implement the FETCH phase. You will have to understand the structure of the memory system, and how the memory system interfaces with the CPU. You will also have to implement all the necessary CPU entities and ISDU controls to be able to successfully fetch the instructions line by line from the on-board memory to the CPU. Note that since you'll not be doing DECODE and EXECUTE during week 1, you don't have to pass the fetched instructions into the ISDU. But instead, you should display the content of the IR, which will be storing the fetched instructions at the end of the FETCH phase.

You are provided with the following entities on the website Mem2IO, Test_Memory, and ISDU. For the first week you do not need to use the Mem2IO, however to remove errors in week 2 there is no harm in using the entity in your design for week 1 as well. The use for Test_Memory is only to simulate your design, to replace the off chip memory. The design you upload to the FPGA should not have Test_Memory, unless it is to debug.

For the purpose of Week 1 demo, you should connect the HEX displays directly to the IR rather than connecting them to the Mem2IO (in contrast, in week 2, you will specify a special address in memory that you write to in order to show data on the HEX displays). To display the content of the IR on the FPGA, there are extra pause states at the end of the FETCH phase to be able to hold and see the content of the IR. Pressing the 'continue' button, your ISDU should loop back to perform the FETCH phase all over again, instead of continuing onto the DECODE phase.

You should not need to modify the given ISDU for week 1, you will be required to create a higher level LC3 entity and begin implementing all the component parts of the LC3 such as the program counter, register file, and memory interface. You are free to implement the top level entity as a schematic or as raw SystemVerilog code.

Week 1 Demo Point Breakdown:

1 point: Simulate the correct value of $MAR = PC$ and $PC = PC + 1$; (use Test_Memory)

1 point: Simulate the correct value of $MDR = M(MAR)$ and $IR = MDR$; (use Test_Memory)

3 points: Correct operation on the FPGA: Displaying correct value of IR on HEX4-7 in state PauseIR1; (Must use physical memory, i.e. do not use Test_Memory)

B. Week 2:

For the second week, you will need to implement the DECODE and the EXECUTE phase. You will first extend the provided skeleton ISDU to include all the necessary state transitions and the necessary inputs/outputs in each of the states.

You will need to learn and understand the specification of the LC3 and its state diagram in order to figure out how to assign the various control signals in each state to produce the desired operations. At this point, you will have to take out the pause states which you have inserted after the FETCH phase during week 1, in order for the ISDU to continue onto the DECODE and the EXECUTE phase instead.

Note: You should not be using Test_Memory in week 2 unless you are simulating or debugging.

Week 2 Demo Point Breakdown:

- 1 point: Basic I/O Test 1
- 1 point: Basic I/O Test 2
- 1 point: Self Modifying Code Test
- 1 point: Multiplication Test
- 1 point: Sort Test
- 1 point: Correct “Act Once” Behavior

IV. LAB

Follow the Lab 6 demo information on the course website. Follow the *Week 2 Test Programs Documentation* in the Lab 6 information page on the course website to demonstrate the 5 tests.

Pin Assignment Table

| Port Name | Location | Comments |
|-----------|----------|--|
| Clk | PIN_Y2 | 50 MHz Clock from the on-board oscillators |
| Run | PIN_R24 | On-Board Push Button (KEY3) |
| Continue | PIN_N21 | On-Board Push Button (KEY2) |
| Reset | PIN_M23 | On-Board Push Button (KEY0) |
| S[0] | PIN_AB28 | On-board slider switch (SW0) |
| S[1] | PIN_AC28 | On-board slider switch (SW1) |
| S[2] | PIN_AC27 | On-board slider switch (SW2) |
| S[3] | PIN_AD27 | On-board slider switch (SW3) |
| S[4] | PIN_AB27 | On-board slider switch (SW4) |
| S[5] | PIN_AC26 | On-board slider switch (SW5) |
| S[6] | PIN_AD26 | On-board slider switch (SW6) |
| S[7] | PIN_AB26 | On-board slider switch (SW7) |
| S[8] | PIN_AC25 | On-board slider switch (SW8) |

| | | |
|---------|----------|--|
| S[9] | PIN_AB25 | On-board slider switch (SW9) |
| S[10] | PIN_AC24 | On-board slider switch (SW10) |
| S[11] | PIN_AB24 | On-board slider switch (SW11) |
| S[12] | PIN_AB23 | On-board slider switch (SW12) |
| S[13] | PIN_AA24 | On-board slider switch (SW13) |
| S[14] | PIN_AA23 | On-board slider switch (SW14) |
| S[15] | PIN_AA22 | On-board slider switch (SW15) |
| LED[0] | PIN_G19 | On-Board LED (LEDR0) |
| LED[1] | PIN_F19 | On-Board LED (LEDR1) |
| LED[2] | PIN_E19 | On-Board LED (LEDR2) |
| LED[3] | PIN_F21 | On-Board LED (LEDR3) |
| LED[4] | PIN_F18 | On-Board LED (LEDR4) |
| LED[5] | PIN_E18 | On-Board LED (LEDR5) |
| LED[6] | PIN_J19 | On-Board LED (LEDR6) |
| LED[7] | PIN_H19 | On-Board LED (LEDR7) |
| LED[8] | PIN_J17 | On-Board LED (LEDR8) |
| LED[9] | PIN_G17 | On-Board LED (LEDR9) |
| LED[10] | PIN_J15 | On-Board LED (LEDR10) |
| LED[11] | PIN_H16 | On-Board LED (LEDR11) |
| HEX0[0] | PIN_G18 | On-Board seven-segment display segment (HEX0[0]) |
| HEX0[1] | PIN_F22 | On-Board seven-segment display segment (HEX0[1]) |
| HEX0[2] | PIN_E17 | On-Board seven-segment display segment (HEX0[2]) |
| HEX0[3] | PIN_L26 | On-Board seven-segment display segment (HEX0[3]) |
| HEX0[4] | PIN_L25 | On-Board seven-segment display segment (HEX0[4]) |
| HEX0[5] | PIN_J22 | On-Board seven-segment display segment (HEX0[5]) |
| HEX0[6] | PIN_H22 | On-Board seven-segment display segment (HEX0[6]) |
| HEX1[0] | PIN_M24 | On-Board seven-segment display segment (HEX1[0]) |
| HEX1[1] | PIN_Y22 | On-Board seven-segment display segment (HEX1[1]) |
| HEX1[2] | PIN_W21 | On-Board seven-segment display segment (HEX1[2]) |
| HEX1[3] | PIN_W22 | On-Board seven-segment display segment (HEX1[3]) |
| HEX1[4] | PIN_W25 | On-Board seven-segment display segment (HEX1[4]) |
| HEX1[5] | PIN_U23 | On-Board seven-segment display segment (HEX1[5]) |
| HEX1[6] | PIN_U24 | On-Board seven-segment display segment (HEX1[6]) |
| HEX2[0] | PIN_AA25 | On-Board seven-segment display segment (HEX2[0]) |
| HEX2[1] | PIN_AA26 | On-Board seven-segment display segment (HEX2[1]) |
| HEX2[2] | PIN_Y25 | On-Board seven-segment display segment (HEX2[2]) |
| HEX2[3] | PIN_W26 | On-Board seven-segment display segment (HEX2[3]) |
| HEX2[4] | PIN_Y26 | On-Board seven-segment display segment (HEX2[4]) |
| HEX2[5] | PIN_W27 | On-Board seven-segment display segment (HEX2[5]) |
| HEX2[6] | PIN_W28 | On-Board seven-segment display segment (HEX2[6]) |
| HEX3[0] | PIN_V21 | On-Board seven-segment display segment (HEX3[0]) |
| HEX3[1] | PIN_U21 | On-Board seven-segment display segment (HEX3[1]) |
| HEX3[2] | PIN_AB20 | On-Board seven-segment display segment (HEX3[2]) |
| HEX3[3] | PIN_AA21 | On-Board seven-segment display segment (HEX3[3]) |
| HEX3[4] | PIN_AD24 | On-Board seven-segment display segment (HEX3[4]) |
| HEX3[5] | PIN_AF23 | On-Board seven-segment display segment (HEX3[5]) |
| HEX3[6] | PIN_Y19 | On-Board seven-segment display segment (HEX3[6]) |
| CE | PIN_AF8 | Chip Enable for SRAM – active low |
| UB | PIN_AC4 | Upper Byte enable for SRAM– active low |
| LB | PIN_AD4 | Lower Byte enable for SRAM – active low |
| OE | PIN_AD5 | Output Enable for SRAM – active low |
| WE | PIN_AE8 | Write Enable for SRAM – active low |
| Data[0] | PIN_AH3 | Bidirectional Data Bus for SRAM - bit 0 |

| | | |
|----------|----------|--|
| Data[1] | PIN_AF4 | Bidirectional Data Bus for SRAM - bit 1 |
| Data[2] | PIN_AG4 | Bidirectional Data Bus for SRAM - bit 2 |
| Data[3] | PIN_AH4 | Bidirectional Data Bus for SRAM - bit 3 |
| Data[4] | PIN_AF6 | Bidirectional Data Bus for SRAM - bit 4 |
| Data[5] | PIN_AG6 | Bidirectional Data Bus for SRAM - bit 5 |
| Data[6] | PIN_AH6 | Bidirectional Data Bus for SRAM - bit 6 |
| Data[7] | PIN_AF7 | Bidirectional Data Bus for SRAM - bit 7 |
| Data[8] | PIN_AD1 | Bidirectional Data Bus for SRAM - bit 8 |
| Data[9] | PIN_AD2 | Bidirectional Data Bus for SRAM - bit 9 |
| Data[10] | PIN_AE2 | Bidirectional Data Bus for SRAM - bit 10 |
| Data[11] | PIN_AE1 | Bidirectional Data Bus for SRAM - bit 11 |
| Data[12] | PIN_AE3 | Bidirectional Data Bus for SRAM - bit 12 |
| Data[13] | PIN_AE4 | Bidirectional Data Bus for SRAM - bit 13 |
| Data[14] | PIN_AF3 | Bidirectional Data Bus for SRAM - bit 14 |
| Data[15] | PIN_AG3 | Bidirectional Data Bus for SRAM - bit 15 |
| ADDR[0] | PIN_AB7 | SRAM address bit 0 |
| ADDR[1] | PIN_AD7 | SRAM address bit 1 |
| ADDR[2] | PIN_AE7 | SRAM address bit 2 |
| ADDR[3] | PIN_AC7 | SRAM address bit 3 |
| ADDR[4] | PIN_AB6 | SRAM address bit 4 |
| ADDR[5] | PIN_AE6 | SRAM address bit 5 |
| ADDR[6] | PIN_AB5 | SRAM address bit 6 |
| ADDR[7] | PIN_AC5 | SRAM address bit 7 |
| ADDR[8] | PIN_AF5 | SRAM address bit 8 |
| ADDR[9] | PIN_T7 | SRAM address bit 9 |
| ADDR[10] | PIN_AF2 | SRAM address bit 10 |
| ADDR[11] | PIN_AD3 | SRAM address bit 11 |
| ADDR[12] | PIN_AB4 | SRAM address bit 12 |
| ADDR[13] | PIN_AC3 | SRAM address bit 13 |
| ADDR[14] | PIN_AA4 | SRAM address bit 14 |
| ADDR[15] | PIN_AB11 | SRAM address bit 15 |
| ADDR[16] | PIN_AC11 | SRAM address bit 16 |
| ADDR[17] | PIN_AB9 | SRAM address bit 17 |
| ADDR[18] | PIN_AB8 | SRAM address bit 18 |
| ADDR[19] | PIN_T8 | SRAM address bit 19 |

V. POST-LAB

1.) Refer to the Design Resources and Statistics in IQT.30-32 and complete the following design statistics table.

| | |
|---------------|--|
| LUT | |
| DSP | |
| Memory (BRAM) | |
| Flip-Flop | |
| Frequency | |
| Static Power | |

| | |
|---------------|--|
| Dynamic Power | |
| Total Power | |

Document any problems you encountered and your solutions to them, and a short conclusion. Before you leave from your lab session submit your latest project code including the .sv files to your TA on his/her USB drive. TAs are under no obligation to accept late code, code that doesn't compile (unless you got 0 demo points) or code files that are intermixed with other project files.

2.) Answer the following questions in the lab report

- What is MEM2IO used for, i.e. what is its main function?
- What is the difference between BR and JMP instructions?

VI. REPORT

You do NOT need to write a report after week 1. Instead you will write one report for the entirety of Lab 6.

In your lab report, should hand in the following:

- An introduction;
- Written description of the operation of your circuit;
- Written purpose and operation of each module, including the inputs/outputs of the modules;
- State diagram for your controller;
- Description of how the instruction sequencer/decoder works. Describe how the control signals from the instruction sequencer/decoder are used to perform proper operations in each state.
- Schematic block diagram with components, ports, and interconnections labeled;
- Annotated pre-lab simulation waveforms. The simulation waveforms should contain at least the complete simulations for one instruction from each of the three instruction categories (ADD/ADDi/AND/ANDi/NOT; MR/JMP/JSR; LDR/STR);
- Design stats ("Total Logic Elements", "Total Registers" and "Max operating frequency")
- Answers to post-lab questions;
- A conclusion regarding what worked and what didn't, with explanations of any possible causes and the potential remedies.